

### Question 1

- a) Structural model
- b) Behavioral model
- c) The models are equivalent as the waveforms verify that both models exhibit the same functionality by yielding the same results when given the same inputs.

Wave - Default


Msgs

/serial\_adder\_tb/ck 0  
 /serial\_adder\_tb/reset 0  
 /serial\_adder\_tb/load 1  
 /serial\_adder\_tb/en... 1  
 /serial\_adder\_tb/A 0101  
 /serial\_adder\_tb/B 0011  
 /serial\_adder\_tb/cout St0  
 /serial\_adder\_tb/SUM 0000

0000 0011  
 0000 0110  
 1000 x100 xx10 1xx1 01xx 101x 1101


Now 130000 ps  
 Cursor 1 13488 ps  
 13488 ps 50000 ps 100000 ps 150000 ps 200000 ps 250000 ps

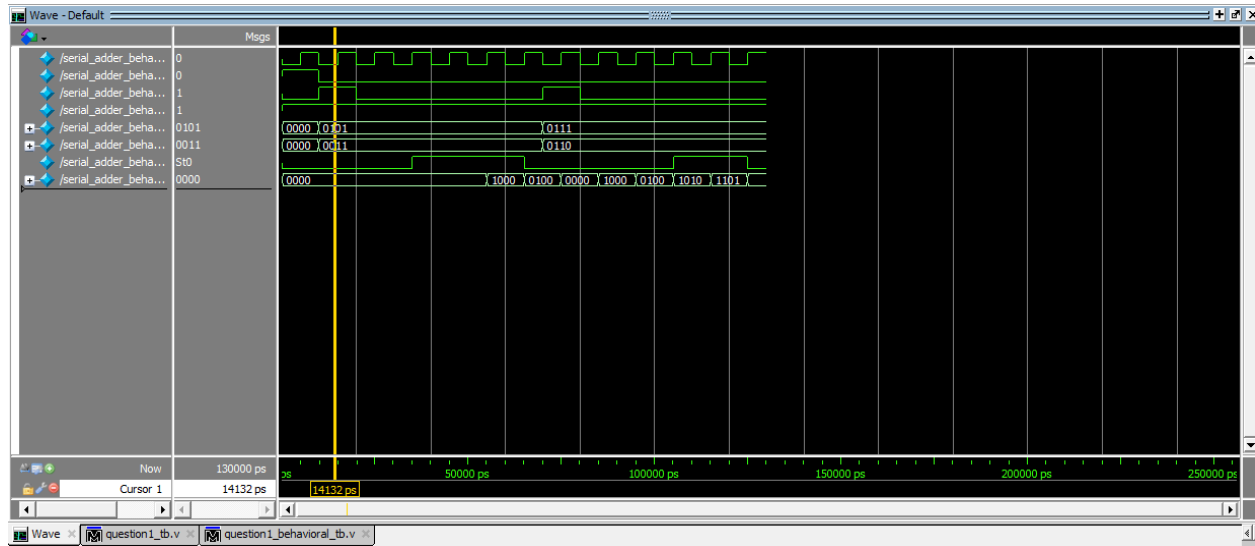*Pictured below: waveform for behavioral*



## Question 2

a) 4 bit CLA

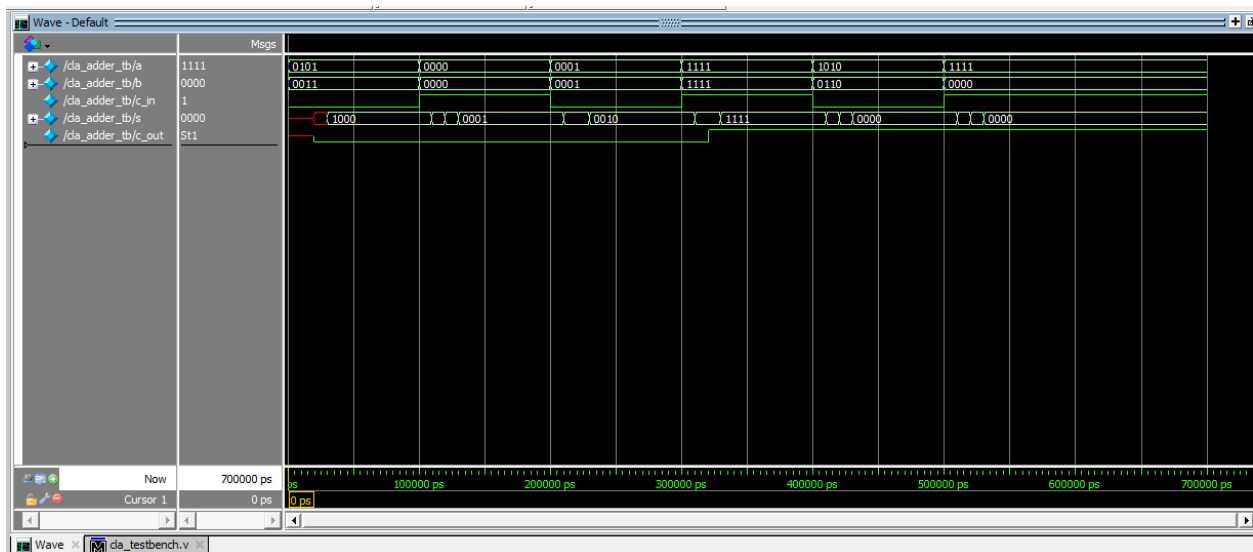

b) Derive an input that exhibits the largest delay from C0 the MSB and find the actual delay:

- The input that has the largest delay is  $a = 1111$ ,  $b = 0000$ , and  $c = 1$ . This is because the carry in must take the longest path to be able to derive the output.
- The typical delay for the tests was about 100,000 ps (100 ns) which was the time to reach the correct result. Compared to the 200,000 ps (200 ns), which was the time for the critical path to be able to derive the appropriate sum and carry out.

c) Simulation output below

```

# T=0 | a=0101 b=0011 c_in=0 | s=xxxx c_out=x
# T=2000 | a=0101 b=0011 c_in=0 | s=xxx0 c_out=0
# T=3000 | a=0101 b=0011 c_in=0 | s=1000 c_out=0
# T=10000 | a=0000 b=0000 c_in=1 | s=1000 c_out=0
# T=11000 | a=0000 b=0000 c_in=1 | s=1001 c_out=0
# T=12000 | a=0000 b=0000 c_in=1 | s=1111 c_out=0
# T=13000 | a=0000 b=0000 c_in=1 | s=0001 c_out=0
# At time 20000: Correct Result: Sum = 0001, Cout = 0
# T=20000 | a=0001 b=0001 c_in=0 | s=0001 c_out=0
# T=21000 | a=0001 b=0001 c_in=0 | s=0000 c_out=0
# T=23000 | a=0001 b=0001 c_in=0 | s=0010 c_out=0
# At time 30000: Correct Result: Sum = 0010, Cout = 0
# T=30000 | a=1111 b=1111 c_in=1 | s=0010 c_out=0
# T=31000 | a=1111 b=1111 c_in=1 | s=0011 c_out=0
# T=32000 | a=1111 b=1111 c_in=1 | s=0011 c_out=1
# T=33000 | a=1111 b=1111 c_in=1 | s=1111 c_out=1
# At time 40000: Correct Result: Sum = 1111, Cout = 1
# T=40000 | a=1010 b=0110 c_in=0 | s=1111 c_out=1
# T=41000 | a=1010 b=0110 c_in=0 | s=1110 c_out=1
# T=42000 | a=1010 b=0110 c_in=0 | s=0010 c_out=1
# T=43000 | a=1010 b=0110 c_in=0 | s=0000 c_out=1
# At time 50000: Correct Result: Sum = 0000, Cout = 1
# T=50000 | a=1111 b=0000 c_in=1 | s=0000 c_out=1
# T=51000 | a=1111 b=0000 c_in=1 | s=0001 c_out=1
# T=52000 | a=1111 b=0000 c_in=1 | s=0010 c_out=1
# T=53000 | a=1111 b=0000 c_in=1 | s=0000 c_out=1
# At time 70000: Correct Result: Sum = 0000, Cout = 1

```